



“Digital IC Design Diploma”

# Asynchronous FIFO

Under the supervision of:

Eng. Ali Eltemsah

Submitted by:

Members	Group
Ahmed Khalaf Mohamed Ali	13

The following snippets are some of the testing scenarios of the functionality of the Asynchronous FIFO

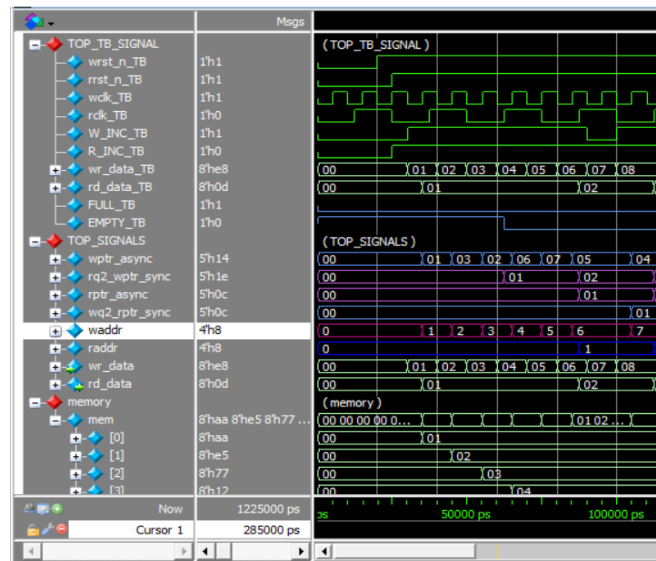


Figure 1: The start of the simulation, reset asserts and deasserts as shown, and shows the empty flag and full flag

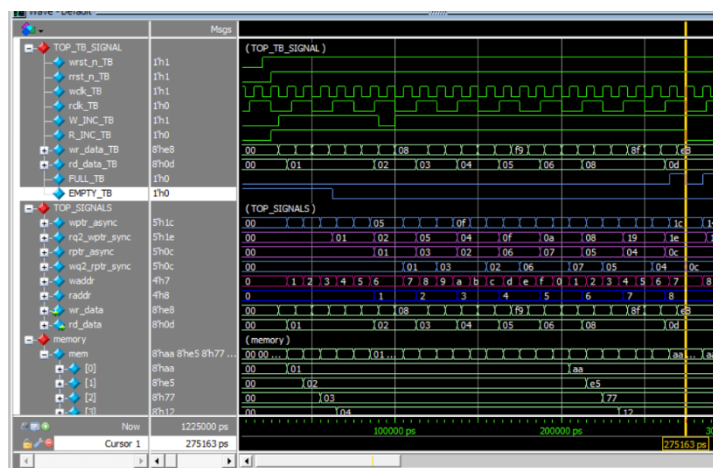


Figure 2: assert read and write enable, and show the data read and the flags behavioral.

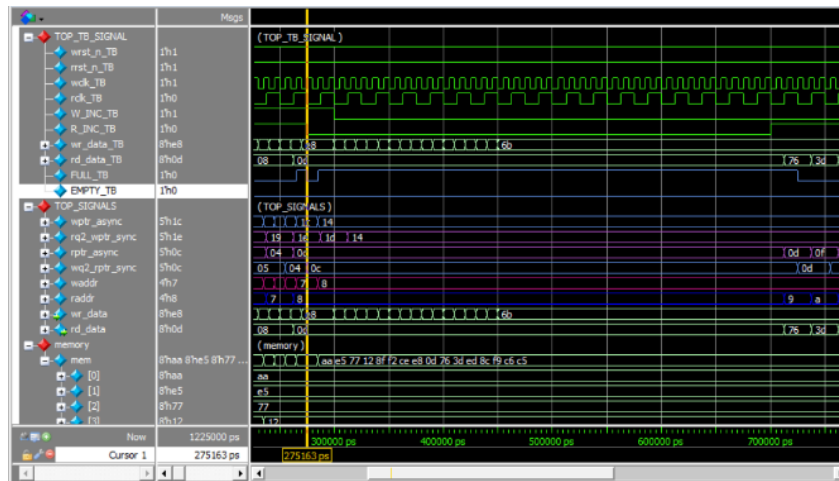


Figure 3: deassert the read and write that do not read the next data and do not change the pointer\_reg.

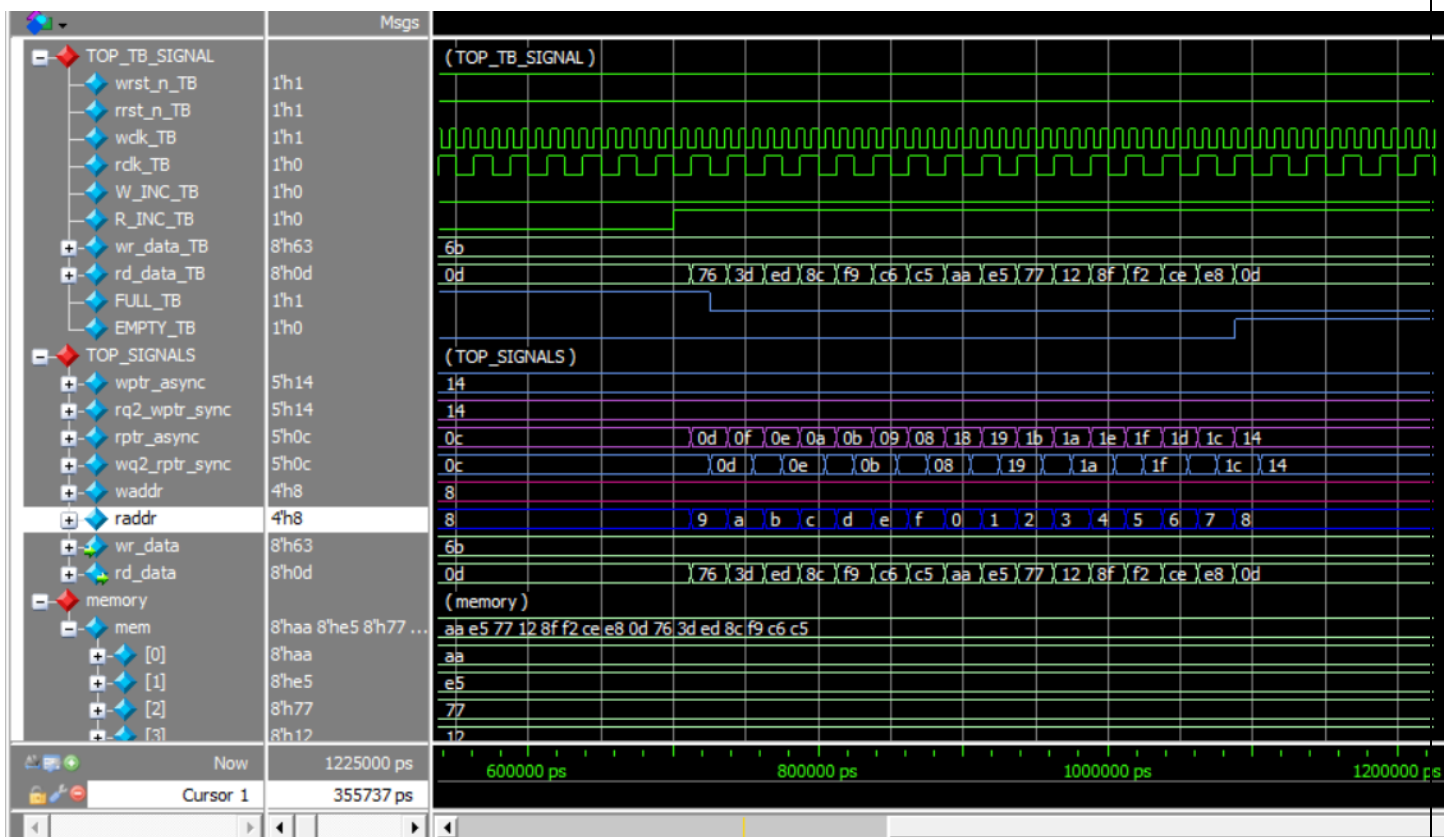


Figure 4: Insert read enable, and after reading, the empty flag should be high.

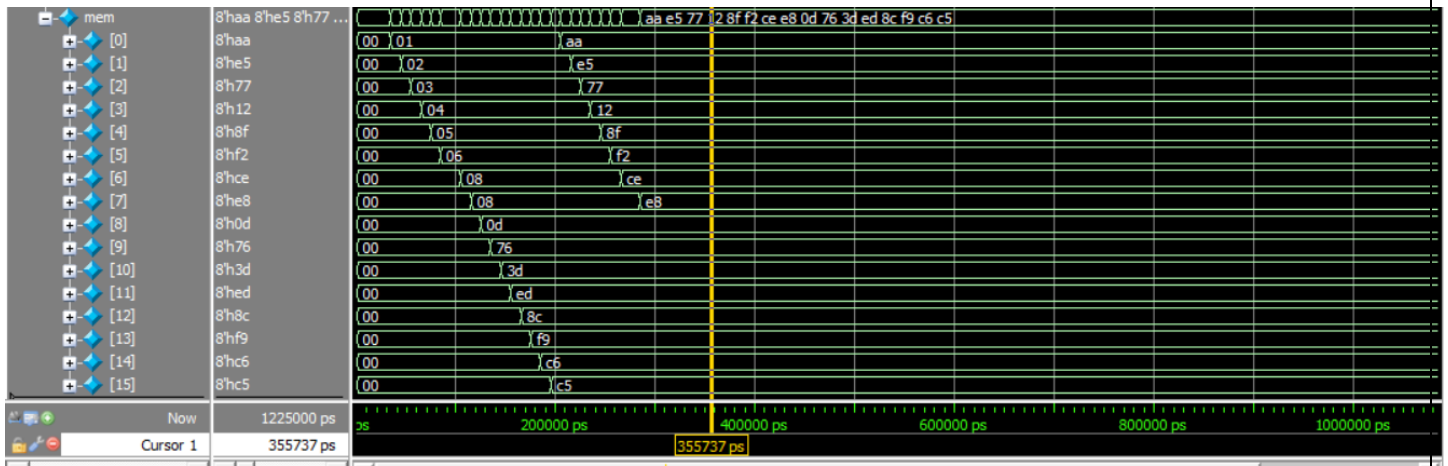


Figure 4: memory values.

```
# Time: 0 ps Iteration: 0 Process: /ASYNC_FIFO_TB/#INITIAL#49 File: ASYNC_FIFO_TB.v Line: 50
# success: FIFO is Full as expected
# success: FIFO is empty as expected
```

Figure 4: memory values.