



“Digital IC Design Diploma”

# Data Synchronizer

Under the supervision of:

Eng. Ali Eltemsah

Submitted by:

Members	Group
Ahmed Khalaf Mohamed Ali	13

The following snippets are some of the testing scenarios of the functionality of the Data Synchronizer:

 


Figure 1: The start of the simulation, reset asserts and deasserts as shown by the yellow pointer

 


Figure 2: insert a5 on a bus and not wait enough time, and another data 5a is gone.

**Note: this must be taken into mind, and the speed of the sender must be slower than the receiver's speed**

**At least three times, or take into account the routing delay.**

 


Figure 3: Insert FF on a bus and enable the bus too much, and the data is transmitted correctly after three cycles.



Figure 4: Insert BA on a bus and do not enable the bus too much; the data is not transmitted.